

① Use
$$U_E = \frac{k_e q_1 q_2}{r} = \frac{(8.9 \times 10^9 \frac{Nm^2}{C^2})(5 \times 10^{-6} C)(-2 \times 10^{-6} C)}{5m} = -1.8 \times 10^{-2} J$$

② To find V , the electric potential, use $V = k_e \frac{Q}{r}$. Since there are two charges, the voltages are added together, or $V_{\text{point a}} = k_e \frac{Q_1}{r_1} + k_e \frac{Q_2}{r_2}$

$$= (8.9 \times 10^9 \frac{Nm^2}{C^2}) \left(\frac{2.5 \times 10^{-9} C}{.05m} + \frac{(-2.5 \times 10^{-9} C)}{.15m} \right) = 300V \text{ at point a.}$$

Also, $V_{\text{point b}} = \frac{k_e}{r_b} (Q_1 + Q_2) = \frac{k_e}{r_b} (2.5 \times 10^{-9} C - 2.5 \times 10^{-9} C) = 0V$
 (distance is the same)

b) Using Work: $q\Delta V = q(V_{\text{point b}} - \infty) = q(0V - 0V) = 0J$, where V_{∞} is the voltage at $r = \infty$.

③ Using the conservation of kinetic and electric potential energies (the only types of energies involved here), we have $K_i + U_{Ei} = K_f + U_{Ef}$, or

(2)

$$K_F = K_i + U_{E_i} - U_{E_f} = K_i - \Delta U_E = K_i - q\Delta V = K_i - (2e)(\Delta V)$$

$$= 1.2 \times 10^{16} \text{ J} - 2(1.6 \times 10^{19} \text{ C})(-0.5 \text{ mV}) = 1.2 \times 10^{17} \text{ J} - 2(1.6 \times 10^{19} \text{ C})(0.5 \times 10^{-3} \text{ V})$$

$$= 2.8 \times 10^{16} \text{ J}$$

(4) a) Let's first find the capacitance, then ΔV , and then E (direction and magnitude). For a parallel plate capacitor, $C = \frac{\epsilon_0 A}{d}$

$$= \frac{(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2})(1 \times 10^{-4} \text{ m}^2)}{(0.25 \times 10^{-3} \text{ m})} = 3.54 \times 10^{-12} \text{ F}$$

Then $\Delta V = \frac{Q}{C} = \frac{4 \times 10^{-12} \text{ C}}{3.54 \times 10^{-12} \text{ F}} = 1.13 \text{ V}$ and $E = \frac{\Delta V}{d} = \frac{1.13 \text{ V}}{0.25 \times 10^{-3} \text{ m}} = 4.52 \times 10^3 \frac{\text{V}}{\text{m}}$

with the direction toward the negative plate.

b) Since ΔV and d doubles, then ΔV also doubles, while E stays the same since it is determined by the ratio of the two.

(5) To find ΔV between the bird's feet, use $\Delta V = IR$. To find R , use $R = \frac{\rho L}{A}$ where A is the cross-sectional area of the wire, or $A = \pi r^2 = \pi(\frac{d}{2})^2$


③ such

where r is the radius and d , the diameter. $S. R = \frac{(2.65 \times 10^{-8} \Omega \cdot m) (\cdot 0.02 m)}{\pi (\frac{0.02 m}{2})^2}$

from p667 of book

that $\Delta V = \frac{(150 A) (2.65 \times 10^{-8} \Omega \cdot m) (\cdot 0.02 m)}{\pi (\frac{0.02 m}{2})^2} = 2.5 \times 10^{-4} V$

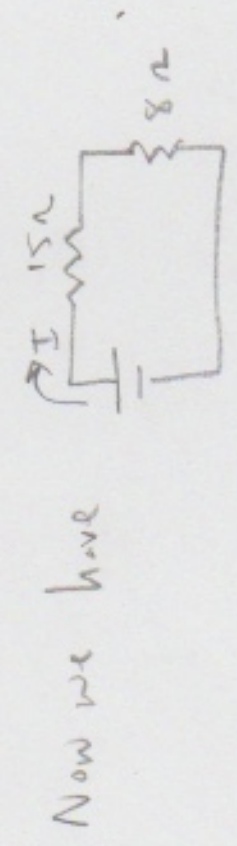⑥ The 12Ω and 24Ω resistors are in parallel so combining them into one equivalent resistor leads to $\frac{1}{R_{eq1}} = \frac{1}{12 \Omega} + \frac{1}{24 \Omega} = \frac{2+1}{24 \Omega} = \frac{3}{24 \Omega} = \frac{1}{8 \Omega}$



$\Rightarrow R_{eq1} = \frac{24 \Omega}{3} = 8 \Omega$

So the 15Ω and 8Ω resistors


are in series. To reduce them to one equivalent resistor, we add them to arrive at $R_{eq} = 15 \Omega + R_{eq1} = 15 \Omega + 8 \Omega = 23 \Omega$.

b) Now that we have simplified the circuit to $\Delta V = I R_{eq}$, we can use $\Delta V = I R_{eq}$ to find I in the circuit, or $\frac{\Delta V}{R_{eq}} = I = \frac{276 V}{23 \Omega} = 12 A$.


4

Since 12Ω resistor is in parallel with the 12Ω resistor, some of the current will pass through the 12Ω and some, the 24Ω . To determine how much respectively, find ΔV across the 12Ω resistor and then use $I_{12\Omega} = \frac{\Delta V_{12\Omega}}{R}$ to find the current through it. First, the voltage drop across both the 12Ω and 24Ω resistors is $\Delta V_{12\Omega} = (12A)(8\Omega) = 96V$ (since they're in parallel, the voltage drop across them is the same). Then $I_{12\Omega} = \frac{96V}{12\Omega} = 8A$ and $I_{24\Omega} = \frac{96V}{24\Omega} = 4A$.

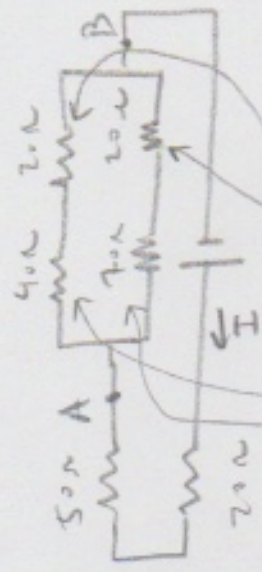7) a) start w
 flows from the battery, find R_{eq} for this circuit first and then invoke Ohm's law.
 To find R_{eq} , the 4Ω and 20Ω resistors are in series as are the 7Ω and 20Ω .




So we have

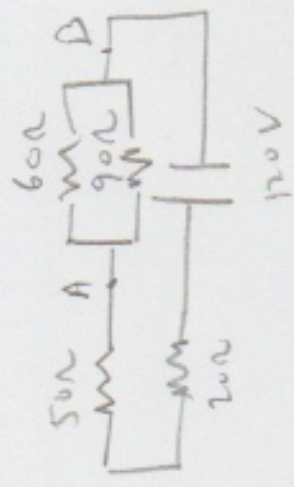

New show "new" 60 ohm and 90 ohm


resistors are in parallel, so $\frac{1}{R_{eq1}} = \frac{1}{60\Omega} + \frac{1}{90\Omega} = \frac{60\Omega}{360\Omega} = \frac{1}{6\Omega} = \frac{1}{R_{eq1}}$

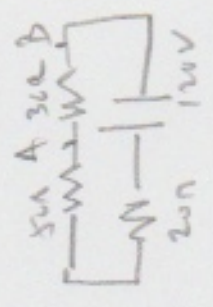$\Rightarrow R_{eq1} = \frac{360\Omega}{10} = 36\Omega$. Then,



All three resistors

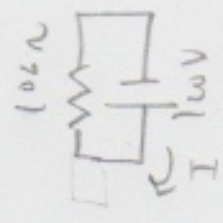are now in series, so $R_{eq} = 20\Omega + 36\Omega = 106\Omega$ and



with $I = \frac{20V}{106\Omega} = 1.13A$,

- b) Since the 36 ohm is the only one between points A and B, then $\Delta V_{AB} = (1.13A)(36\Omega) = 40.75V$ current is flow from the battery until point A.
- c) At the junction point right after A, the current splits. How does

(6)

It split 7. Well, the current through the top wire (branch) is

$$\frac{40.75V}{60\Omega} = 0.68A \quad \text{and through the bottom wire is } \frac{40.75V}{70\Omega} = 0.58A.$$

d) Use Power = $I^2 R = (0.68A)^2 (40\Omega) = 18W.$